
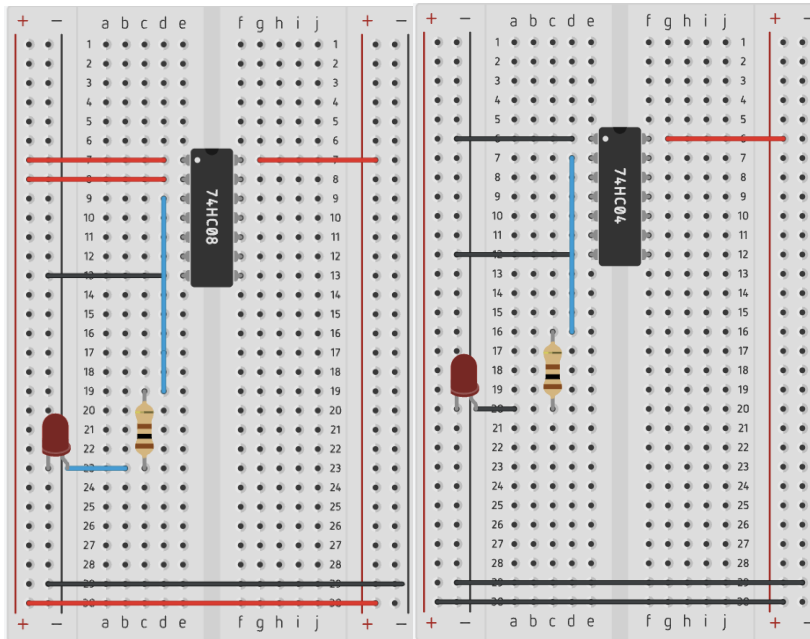


Logic Design Summary Sheet

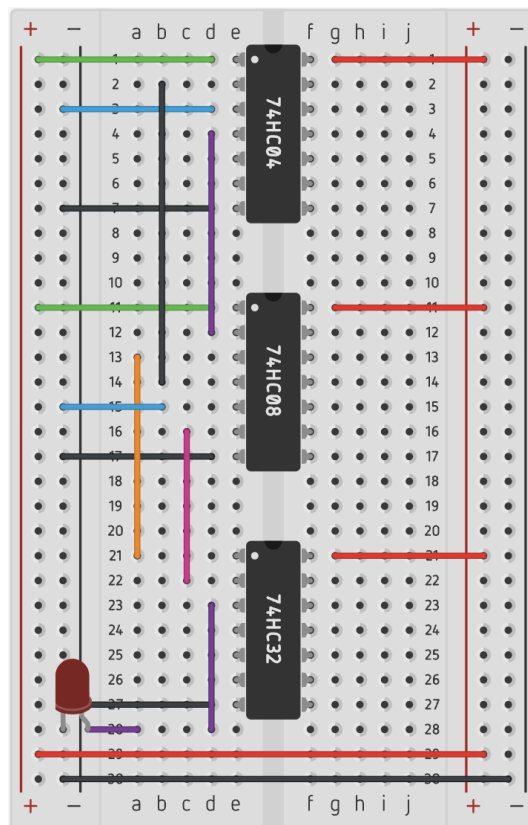Implemented Circuit for AND + OR Gate and NOT Gate:



Implemented Combinational Circuit(XOR):



The inputs are A(Green) and B(Blue). Changing input A means changing both green wires and the same goes for the Blue wire.